



BLG 231E - Digital Circuits

Assignment 2

Due Date: Thursday, November 19, 2020, 23:59.

- Please **write and draw neatly**.
- Please prepare your homework using a computer. Points will be taken off for handwritten submissions.
- **Consequences of plagiarism:** Any cheating will be subject to disciplinary action.
- **No late submissions** will be accepted.
- **Submissions:** Submit your solution PDFs to Ninova. Please **write your full name** (first name and last name) **and Student ID** into your solution PDFs.

If you have any questions, please e-mail **Kıymet Kaya** (kayak16@itu.edu.tr).

1. The truth table for a function $y(A, B, C, D)$ is given below:

	A	B	C	D	y
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	1

- Write the expressions of y in the first and second canonical forms.
- Minimize the expression in the first canonical form using axioms and theorems of Boolean algebra. Show all steps in your minimization and write the name of the axiom/theorem/property you use on the right-hand side of the expression at each step.
- Draw the circuit for the minimized expression in (b) using 2-input NAND gates only. Show all steps and explain your work leading up to the final circuit.