

BLG231E – Assignment 2

Name – Surname: Ö. Malik Kalembaşı

Student ID: 150180112

CRN: 11623

1.

first canonical form of y;

“true” (1) combinations: 0001 0011 0101 1001 1010 1100 1110 1111

sum of minterms: $F(A, B, C, D) = A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABCD$

second canonical form of y;

“false” (0) combinations : 0000 0010 0100 0110 0111 1000 1011 1101

product of maxterms: $F(A, B, C, D) = (A+B+C+D)(A+B+C'+D)(A+B'+C+D)(A+B'+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C'+D')(A'+B'+C+D')$

2.

$F(A, B, C, D) = A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABCD$

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABCD$ (idempotence)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABCD + ABCD'$ (distributivity)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABC(D + D')$ (inverse)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABC(1)$ (identity)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABC$ (idempotence)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABC'D' + ABCD' + ABC + ABCD'$ (distributivity)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABD'(C' + C) + ABC + ABCD'$ (inverse)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABD'(1) + ABC + ABCD'$ (identity)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABD' + ABC + ABCD'$ (commutative)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + AB'CD' + ABCD' + ABD' + ABC$ (distributivity)


$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + ACD'(B' + B) + ABD' + ABC$ (inverse)

$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + ACD'(1) + ABD' + ABC$ (identity)


$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + ACD' + ABD' + ABC$ (idempotence)


$A'B'C'D + A'B'CD + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(distributivity)
$A'B'D(C' + C) + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(inverse)
$A'B'D(1) + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(identity)
$A'B'D + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(idempotence)
$A'B'D + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D + A'B'C'D$	(commutative)
$A'B'D + A'B'C'D + A'BC'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(distributivity)
$A'B'D + A'C'D(B' + B) + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(inverse)
$A'B'D + A'C'D(1) + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(identity)
$A'B'D + A'C'D + AB'C'D + ACD' + ABD' + ABC + A'B'C'D$	(commutative)
$A'B'D + A'C'D + A'B'C'D + AB'C'D + ACD' + ABD' + ABC$	(distributivity)
$A'B'D + A'C'D + B'C'D(A' + A) + ACD' + ABD' + ABC$	(inverse)
$A'B'D + A'C'D + B'C'D(1) + ACD' + ABD' + ABC$	(identity)
$A'B'D + A'C'D + B'C'D + ACD' + ABD' + ABC$	(commutative)
$ABC + ABD' + ACD' + A'B'D + A'C'D + B'C'D$	(final expression)

3.

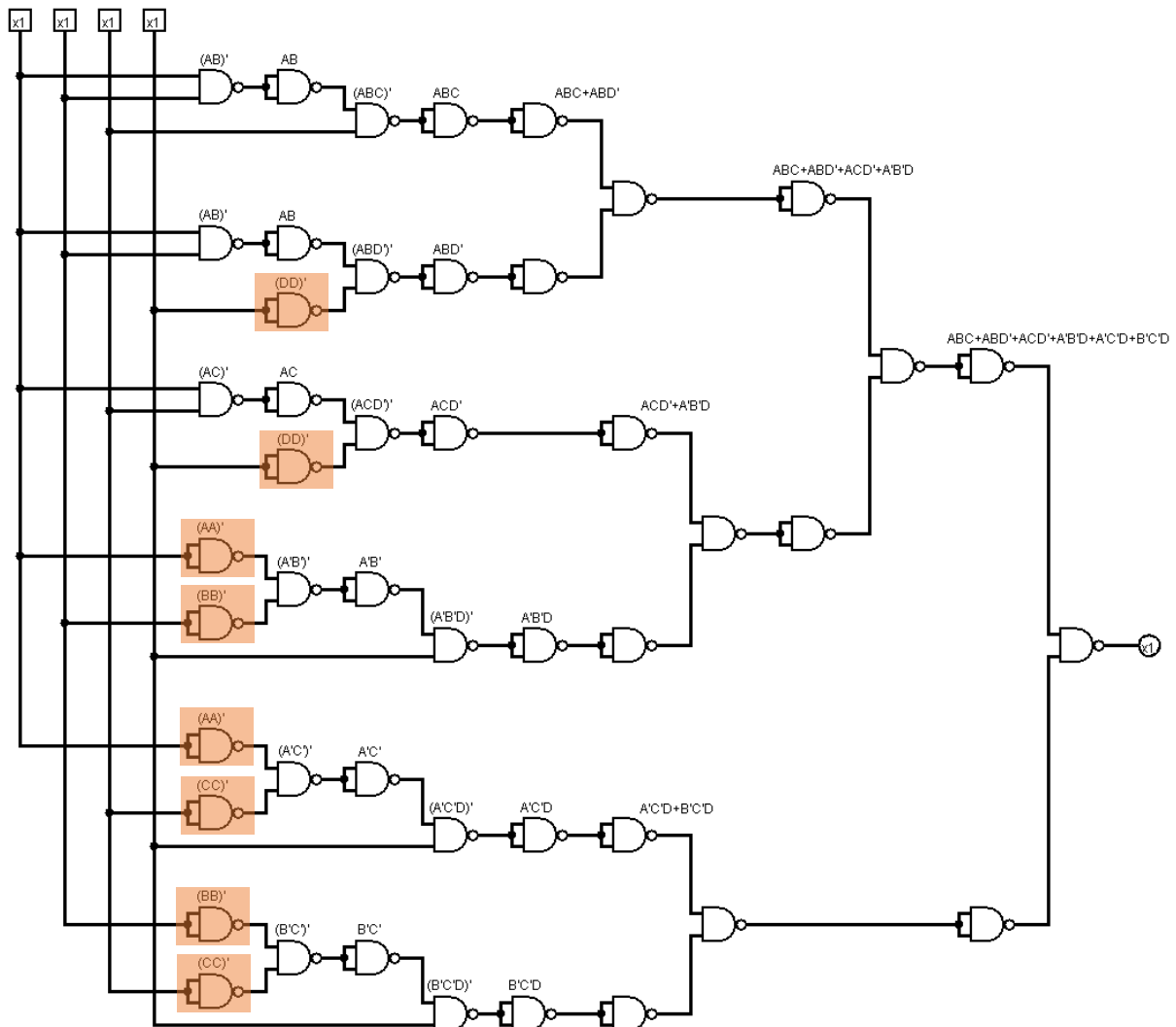


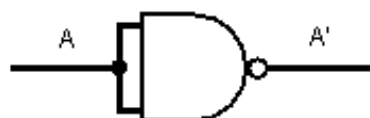
the red filled areas in the circuit work as “NOT gates”.



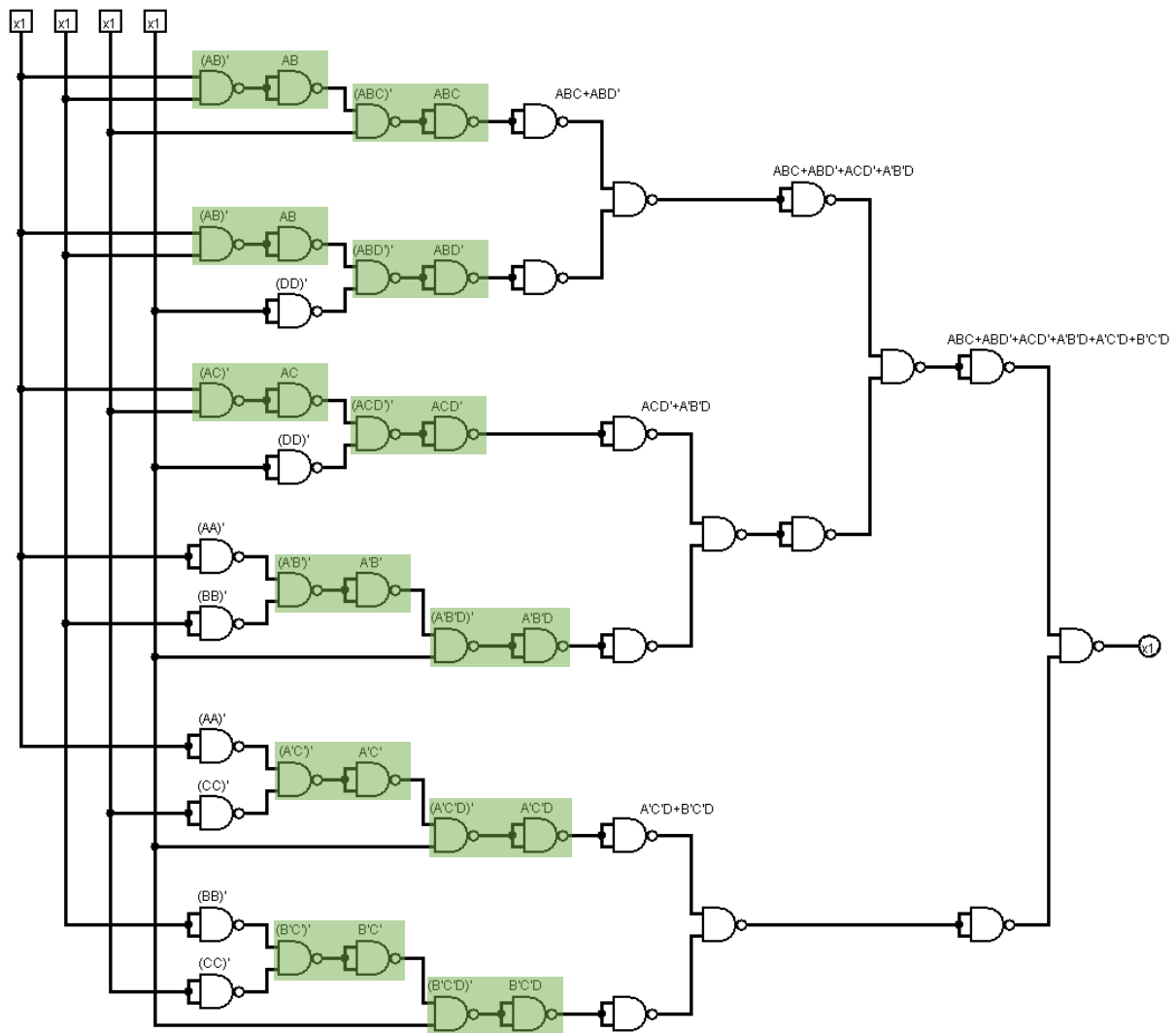

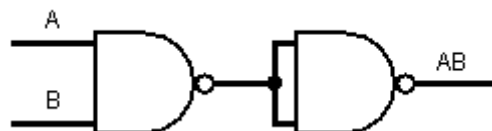the green filled areas in the circuit work as “AND gates”.



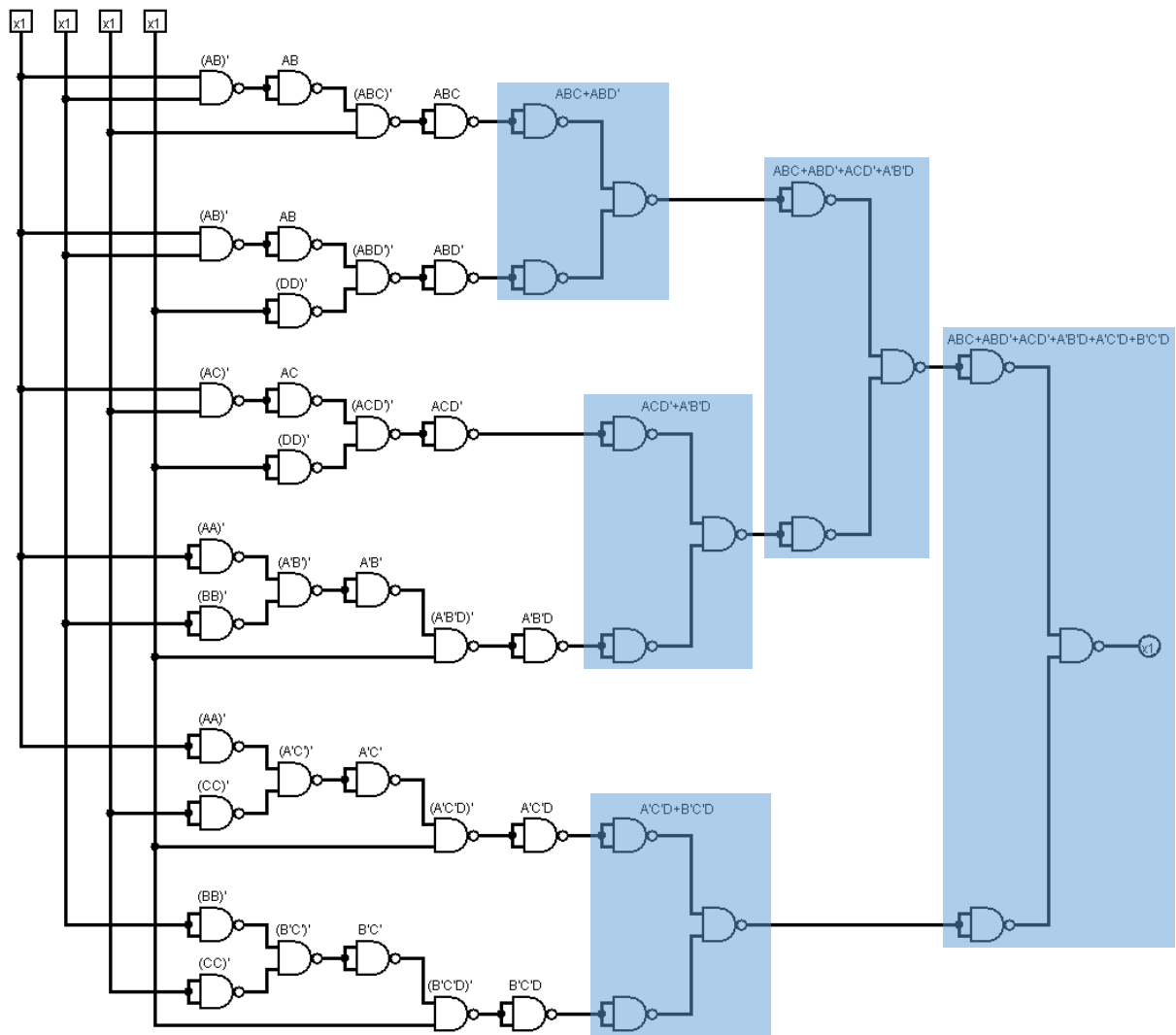

blue filled areas in the circuit work as “OR gates”.

